



Exercise 4

Table 4.1

Parameter Symbol	Parameter Description	Typical Parameter Value		Units
		n-Channel	p-Channel	
V_{T0}	Threshold voltage($V_{BS}=0$)	0.7	-0.8	V
K	Transconductance parameter(in saturation)	134	50	$\mu\text{A}/\text{V}^2$
γ	Bulk threshold parameter	0.45	0.4	$\text{V}^{1/2}$
λ	Channel length modulation parameter	0.1	0.2	V^{-1}
$2 \phi_F $	Surface potential at strong inversion	0.9	0.8	V

* $K = \mu C_{OX}$

- 4-1 For the circuit in Fig.4.1(a) assume that there are no capacitance parasitics associated with M1. The voltage source v_{in} is a small-signal value, whereas voltage source V_{DC} has a dc value of 3 V. Design M1 to achieve the asymptotic frequency response shown in Fig.4.1(b).

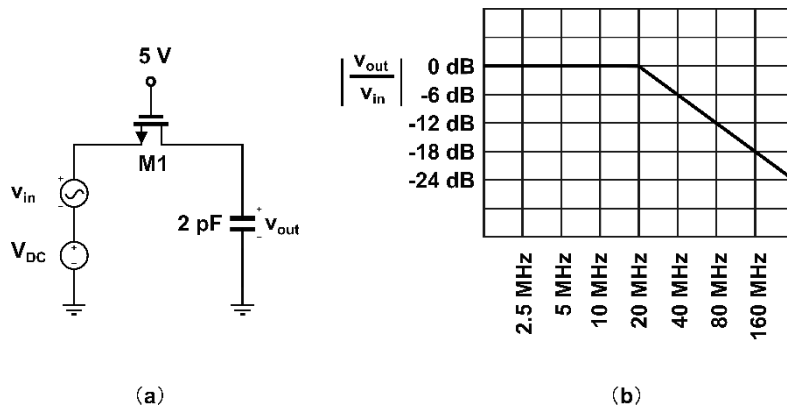


Fig.4.1

Answer:

$f(-3\text{dB}) = 20\text{MHz}$, thus $\omega = 40\pi\text{M rad/s}$. Note that since no dc current flows through the transistor, the dc value of the drain-source voltage is zero.

$$r_{ON} = \frac{L}{KW(V_{GS} - V_T)}, \text{ then } \frac{1}{RC} = \frac{KW(V_{GS} - V_T)}{LC} \text{ find } \frac{W}{L} = \frac{C \times 40\pi \times 10^6}{K(V_{GS} - V_T)}$$

$$V_T = V_{T0} + \gamma \left(\sqrt{2\phi_F + |v_{bs}|} - \sqrt{2\phi_F} \right) = 0.7 + 0.45 \times (\sqrt{0.9 + 3} - \sqrt{0.9}) = 1.16$$

$$\frac{W}{L} = \frac{2 \times 10^{-12} \times 40\pi \times 10^6}{134 \times 10^{-6} \times (2 - 1.16)} = 2.23$$

$$V_t = 0.7, \quad w/l = 2.88$$

4-2 Fig.4.2 illustrates a source-degenerated current source. M1 with $W/L=2\mu/1\mu$, $I_D = 10\mu A$.

- (a) Using Table 4.1 model parameters, calculate the output resistance at the given current bias. Ignore the body effect.
- (b) Calculate the minimum output voltage required to keep the device in saturation.


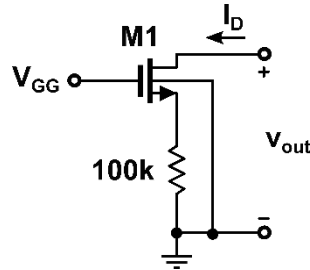


Fig.4.2

Answer:

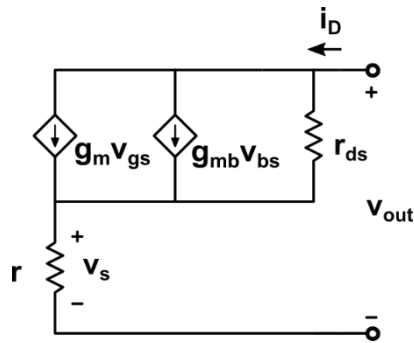The small-signal model of this circuit is shown below



(a) $V_S = I_D \times r = 1V, r_{out} = r + r_{ds} + [(g_m + g_{mb})r_{ds}]r.$

$$g_m = \sqrt{2 \times \frac{KW}{L} I_D} = 73.2 \times 10^{-6}$$

$$g_{mb} = g_m \frac{\gamma}{2(2|\Phi_F| + V_{SB})^{\frac{1}{2}}} = 11.9 \times 10^{-6}$$

$$g_{ds} = \lambda I_D = 1 \times 10^{-6}$$

$$r_{ds} = \frac{1}{g_{ds}} = 1 \times 10^6$$

$$\text{thus } r_{out} = 9.61 \times 10^6$$

(b) $V_T = V_{T0} + \gamma(\sqrt{2|\Phi_F| + |v_{bs}|} - \sqrt{2|\Phi_F|}) = 0.89V. V_{GS} = \left(\sqrt{2 \times \frac{L}{KW} I_D} + V_T\right) =$

$$1.16V. V_{GG} = V_{GS} + V_S = 2.16V, V_{out} > V_{GG} - V_T = 1.27V$$

- 4-3 Calculate the output resistance and the minimum output voltage, while maintaining all devices in saturation, for the circuits shown in Fig.4.3. Assume that i_{OUT} is actually $10\mu A$. Use Table 4.1 for device model information.

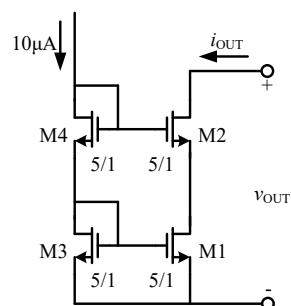


Fig .4.3

Answer:

$$V_{GS3} = V_{GS4} = \left(\sqrt{2 \times \frac{L}{KW} I_D} + V_T \right) = 0.17 + 0.7 V = 0.87 V.$$

$$g_{m2} = g_{m4} = \sqrt{2 \times \frac{KW}{L} I_D} = 115.8 \times 10^{-6}$$

$$r_{out} = r_{ds1} + r_{ds2} + g_{m2} r_{ds1} r_{ds2}.$$

$$r_{ds1} = r_{ds2} = \frac{1}{\lambda I_D} = 1 \times 10^6$$

$$r_{out} = 117.8 \times 10^6$$

$$v_{out} = V_{GS3} + V_{GS4} - V_{T2} = 1.04 V$$

- 4-4 A reference circuit is shown in Fig.4.4, assume that $(W/L)_1=(W/L)_2=(W/L)_3=4$, $(W/L)_4=1$, please derive a symbolic expression of V_{REF} . (已知各管处于饱和区且各管阈值电压为 V_{Ti})

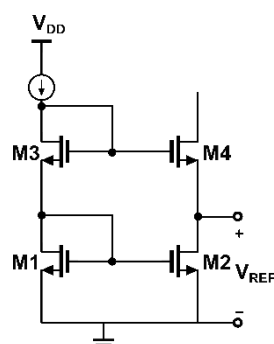


Fig.4.4

Answer:

$$V_{REF} = V_{GS1} + V_{GS3} - V_{GS4}$$

$$V_{REF} = V_{ON1} + V_{T1} + V_{ON3} + V_{T3} - V_{ON4} - V_{T4}$$

$$V_{T3} = V_{T4}$$

$$V_{ON4} = 2 \times V_{ON1} = 2 \times V_{ON3}$$

$$V_{REF} = V_{T1}$$

4-5 As the circuits shown in Fig.4.5, $I_{REF}=0.3\text{mA}$ and $\gamma=0$. Using the model parameters in Table 4.1,

- Calculate the voltage V_b when $V_X=V_Y$;
- If V_b is 100mV smaller than the value in (a), calculate the deviation of I_{out} from 300 μA .

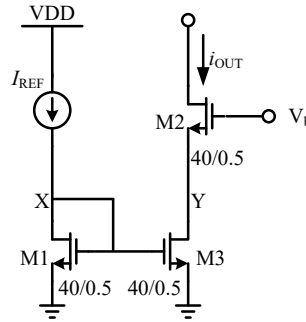


Fig.4.5

Answer:

$$(a) \quad V_{GS1} = \left(\sqrt{2 \times \frac{L}{KW} I_{REF}} + V_T \right) = 0.24 + 0.7 = 0.94 \text{ V}. V_b = 2 \times V_{GS1} = 1.88 \text{ V}.$$

$$(b) \quad \lambda(L = 0.5\mu) = 2 \times \lambda(L = 1\mu) = 0.2\text{V}^{-1}$$

$$I_{out} = I_{REF} \frac{1 + \lambda(V_{GS1} + \Delta V_b)}{1 + \lambda V_{GS1}}, \quad \Delta I_{out} = I_{REF} \frac{\lambda \Delta V_b}{1 + \lambda V_{GS1}} = -5.05 \times 10^{-6}$$

4-6 Design M3 and M4 of Fig.4.6(a) so that the **output characteristics** are identical to the circuit shown in Fig.4.6(b). It is desired that i_{OUT} is ideally 10uA.

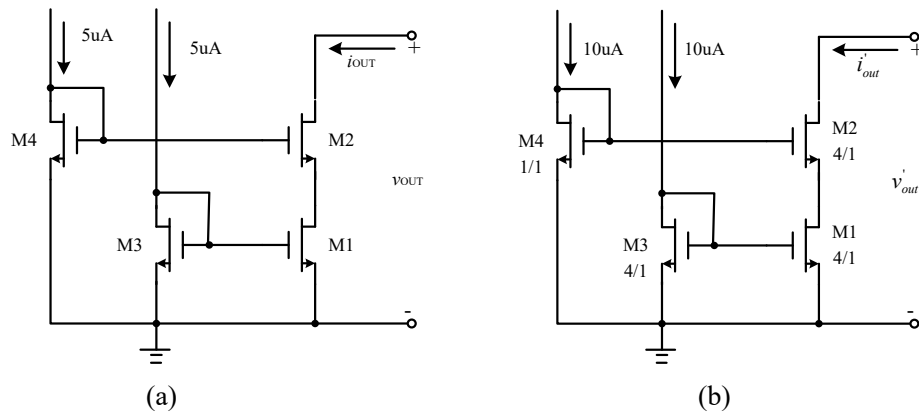


Fig.4.6

$$(a) \quad V_{GS1} = V_{GS3}, V_{GS2} = V_{GS4}. I_3 = I_4 = 5\mu\text{A}, I_{out} = 10\mu\text{A}, \text{ we must have } \left(\frac{W}{L} \right)_1 = 2 \times$$

$$\left(\frac{W}{L} \right)_3, \left(\frac{W}{L} \right)_3 = 2/1.$$

$$\text{In (b) } i_3 = i_4 = 10\mu\text{A} = i_1, \quad \left(\frac{W}{L} \right)_4 \times V_{Dsat4}^2 = \left(\frac{W}{L} \right)_1 \times V_{Dsat1}^2, V_{Dsat4} = 2 \times V_{Dsat1}$$

$$V_{GS4} = V_T + V_{Dsat4}, V_{GS2} = V_T + V_{Dsat4}, V_{out} > V_{GS2} - V_T = V_{Dsat4} = 2 \times V_{Dsat1}$$

$$\text{In (a) } I_3 = I_4 = 5\mu A = 2 \times I_1, \left(\frac{W}{L}\right)_4 \times V_{Dsat4}^2 = \frac{1}{2} \left(\frac{W}{L}\right)_1 \times V_{Dsat1}^2$$

$$\text{because, } \frac{V_{Dsat4}}{V_{Dsat1}} = \sqrt{\frac{1}{2} \times \left(\frac{W}{L}\right)_1 / \left(\frac{W}{L}\right)_4} = 2, \left(\frac{W}{L}\right)_4 = \frac{1}{8} \times \left(\frac{W}{L}\right)_1 = 1/2$$