



Exercise 1

- Two layouts of n-channel MOSFET are shown in Fig.3.1. What is the width and length of the two devices?


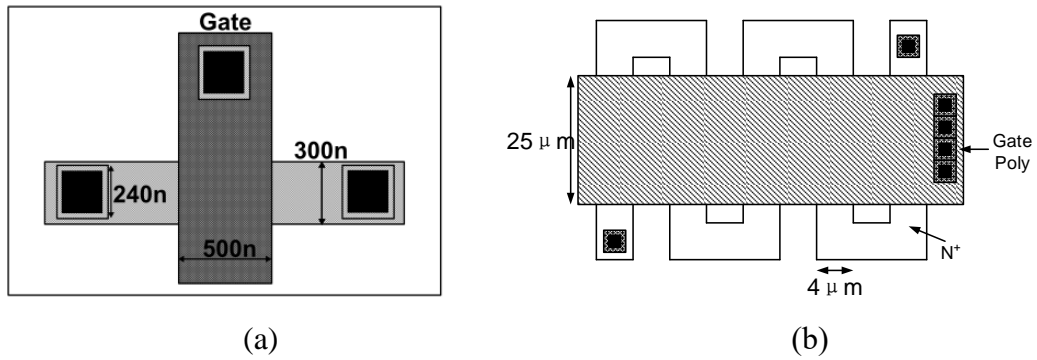


Fig.3.1

- The layouts of a circuit are shown in Fig.3.2. Give the corresponding schematics and its function, and mark the W/L sizes of each transistor. Assume $L=2\lambda$, $\lambda=0.4\mu\text{m}$.

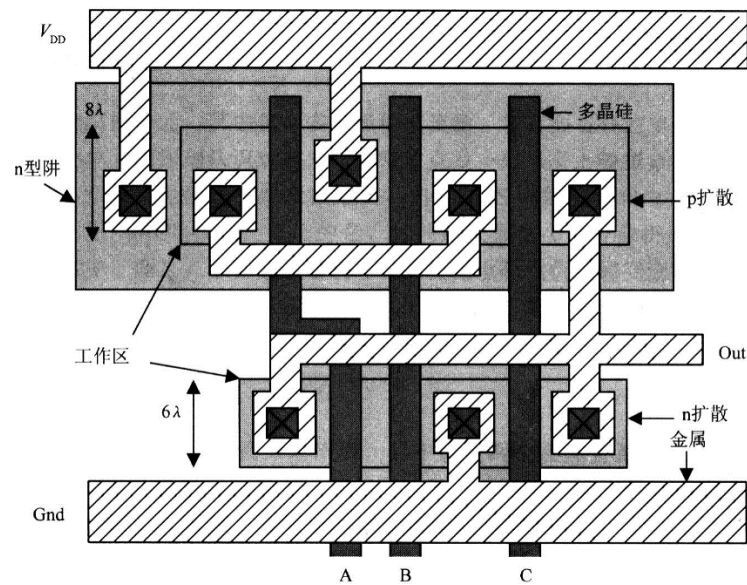

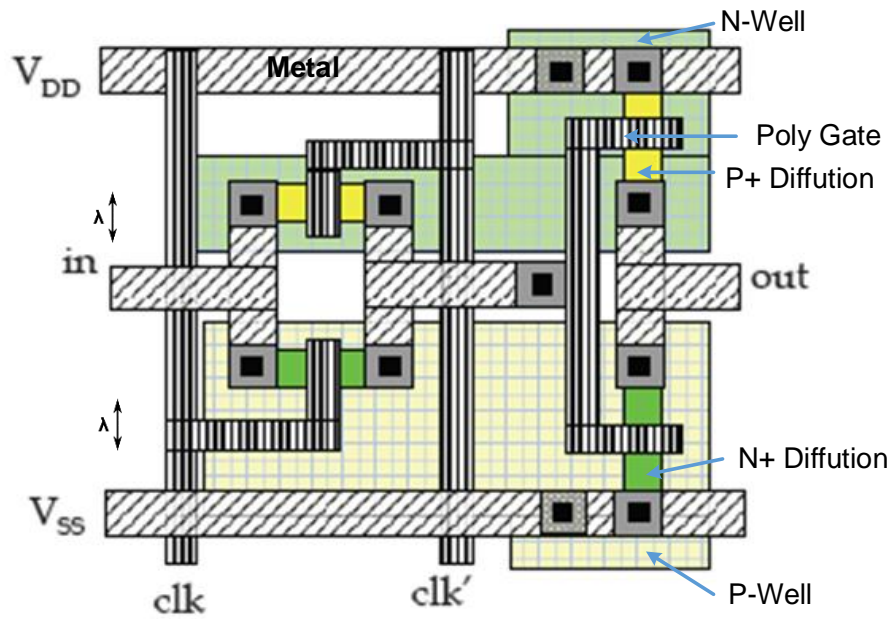


Fig.3.2

3. Layout of a different pair with PMOS current source loads in p-sub N-well technology is shown as Fig.3.3. Give the corresponding schematics and mark the W/L sizes of each transistor. Assume $\lambda=0.4\mu\text{m}$.

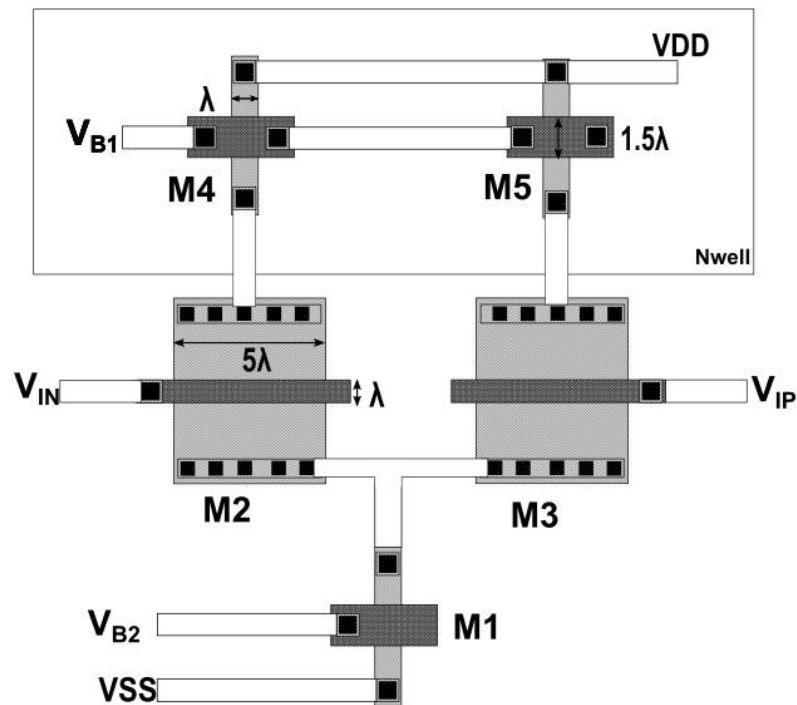


Fig.3.3