



Table 6.1

Parameter Symbol	Parameter Description	Typical Parameter Value		Units
		n-Channel	p-Channel	
V_{T0}	Threshold voltage($V_{BS}=0$)	0.7	-0.8	V
K	Transconductance parameter(in saturation)	134	50	$\mu\text{A}/\text{V}^2$
γ	Bulk threshold parameter	0.45	0.4	$\text{V}^{1/2}$
λ	Channel length modulation parameter	0.1	0.2	V^{-1}
$2 \phi_F $	Surface potential at strong inversion	0.9	0.8	V

$$K = \mu C_{OX}$$

6.1 Calculate the differential transconductance g_{md} and the differential voltage gain A_v of an n-channel input differential amplifier shown in Figure 6.1 , with the parameters shown in table 6.1. Consider $I_{SS}=100\mu\text{A}$ (the drain current of M5), and $W_1/L_1=W_2/L_2=W_3/L_3=W_4/L_4=1$. Assuming all the channel lengths are equal to $1\mu\text{m}$, and $V_{DD}=5\text{V}$. If $W_1/L_1=W_2/L_2=10W_3/L_3=10W_4/L_4=10$, repeat the calculation

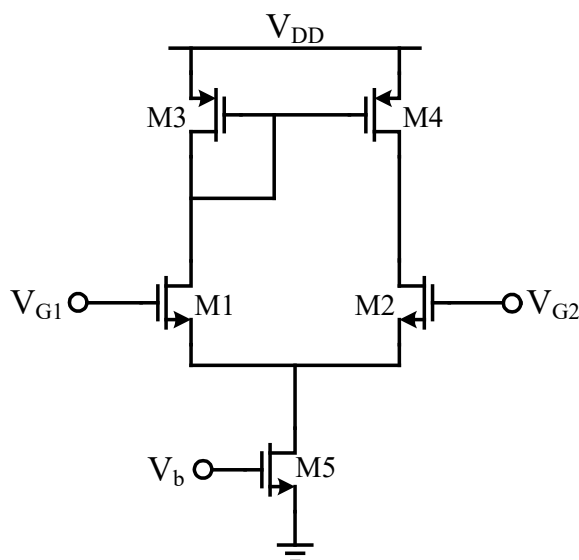


Figure 6.1

6.2 Calculate the maximum($V_{IC(max)}$) and the minimum input common-mode voltages ($V_{IC(min)}$), and the input common mode voltage range (ICMR) of an n-channel input differential amplifier shown in Figure 6.1, with the parameters shown in table 6.1. Assume all MOSFETs are in saturation, all the $(W/L)_i$ are equal to $10\mu\text{m}/1\mu\text{m}$, $I_{SS}=10\mu\text{A}$, and $V_{DD}=5\text{V}$.

6.3 Find the value of the unloaded differential-transconductance, g_{md} , and the unloaded differential-voltage gain, A_v , for the p-channel input differential amplifier of Figure 6.2 when $I_{SS}=10\mu A$ and $I_{SS}=1\mu A$. What is the slew rate of the differential amplifier if a 100 pF capacitor is attached to the output? Assuming $W_1/L_1=W_2/L_2=W_3/L_3=W_4/L_4=1$, and all the channel lengths are equal to $1\mu m$. Use the transistor parameters of Table 6.1.

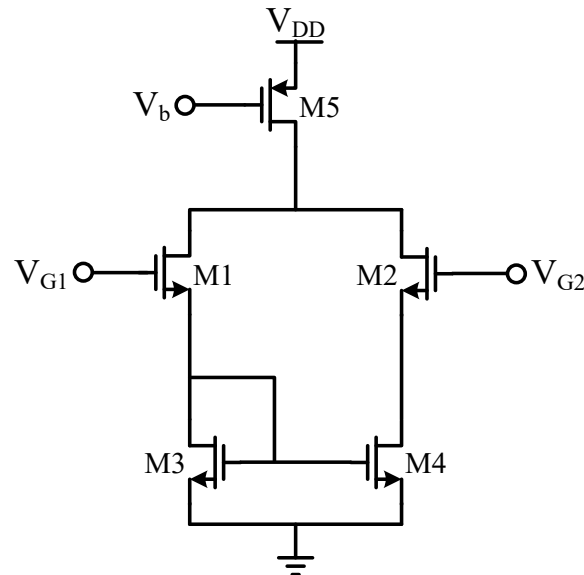


Figure 6.2

6.4 In the circuit of Fig 6.3, assume that $I_{SS}=1mA$, $V_{DD}=3V$ and $W/L=50/0.5$ for all the transistors. And $I_{D5}=I_{D6}=0.8(I_{SS}/2)$. Assuming $\lambda \neq 0$.

- Determine the voltage gain.
- Calculate V_b .
- If I_{SS} requires a minimum voltage of 0.4V, what is the maximum differential output swing?

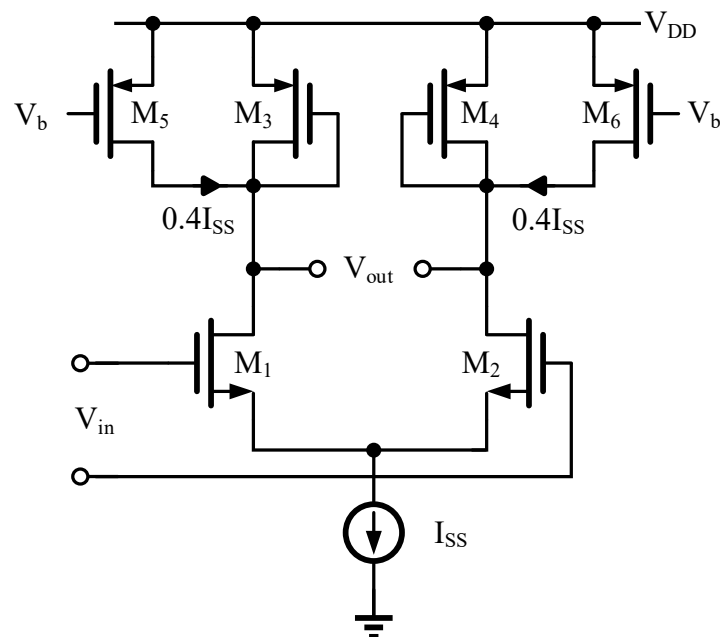


Figure 6.3

6.5 The circuit shown in Figure 6.4 called a folded-current mirror differential amplifier and is useful for low values of power supply. Assume that all W/L values of each transistor is 100. Using the parameters shown in table 6.1,

- Find the maximum input common mode voltage, $V_{IC(max)}$ and the minimum input common mode voltage, $V_{IC(min)}$. Keep all transistors in saturation for this problem.
- What is the input common mode voltage range, ICMR?
- Find the **small signal** voltage gain, v_{out}/v_{in} , if $v_{in} = v_1 - v_2$.

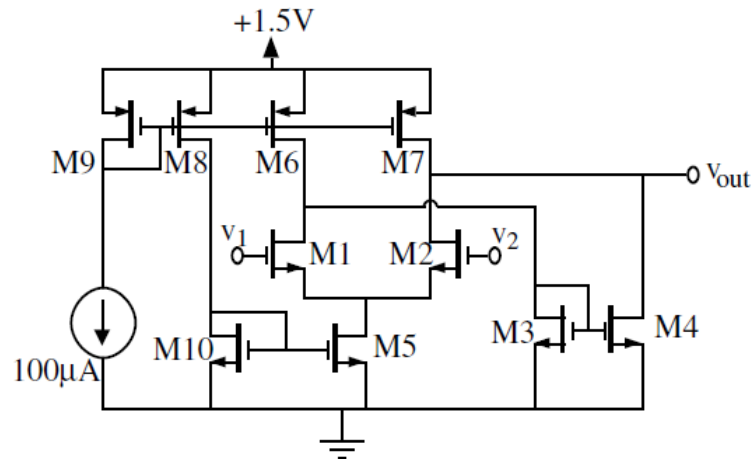


Figure 6.4

6.6 In the circuit of Fig 6.5, assume that $I_{SS} = 0.5\text{mA}$, $V_{DD} = 3\text{V}$, $(W/L)_{1,2} = 50/0.5$ and $(W/L)_{3,4} = 10/0.5$. I_{SS} current is provided by NMOS, and its W/L = 50/0.5. Assuming $\lambda \neq 0$.

- Calculate the range of input common mode voltage.
- If $V_{in,CM} = 1.5\text{V}$, draw a sketch of the small signal differential voltage gain of the circuit when V_{DD} changes from 0 to 3V.
- If the mismatch threshold voltage of M_1 and M_2 is 1mV, calculate CMRR.
- If the $W_3 = 10\mu\text{m}$ and $W_4 = 11\mu\text{m}$, calculate CMRR.

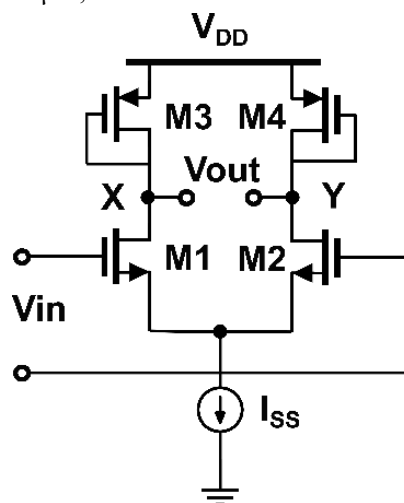


Figure 6.5