



Table 5.1

Parameter Symbol	Parameter Description	Typical Parameter Value		Units
		n-Channel	p-Channel	
V_{T0}	Threshold voltage($V_{BS}=0$)	0.7	-0.8	V
K	Transconductance parameter(in saturation)	134	50	$\mu\text{A}/\text{V}^2$
γ	Bulk threshold parameter	0.45	0.4	$\text{V}^{1/2}$
λ	Channel length modulation parameter	0.1	0.2	V^{-1}
$2 \phi_F $	Surface potential at strong inversion	0.9	0.8	V

$$K = \mu C_{OX}$$

5.1 Assume that W/L ratios of Figure 5.1 are $(W/L)_1 = 2\mu\text{m}/1\mu\text{m}$ and $(W/L)_2 = (W/L)_3 = (W/L)_4 = 1\mu\text{m}/1\mu\text{m}$. Find the dc value of v_{IN} that will give a dc current in M1 of $110\mu\text{A}$. Calculate the small signal voltage gain and output resistance using the parameters of Table 5.1. Assume $\lambda=\gamma=0$.

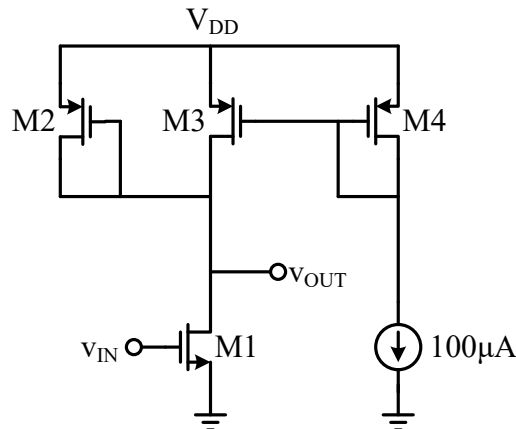


Figure 5.1

5.2 Suppose the common-source stage of Fig 5.2 is to provide an output swing from 1V to 2.5V. Assume that $(W/L)_1 = 50/0.5$, $R_D = 2\text{k}\Omega$, $V_{DD} = 3\text{V}$ and $\lambda = 0$. Use model parameters in Table 5.1.

- Calculate the input voltages that yield $V_{out} = 1\text{V}$ and $V_{out} = 2.5\text{V}$.
- Calculate the drain current and the transconductance of M_1 for both cases.
- How much does the small-signal gain, $g_m R_D$, vary as the output goes from 1V to 2.5V?

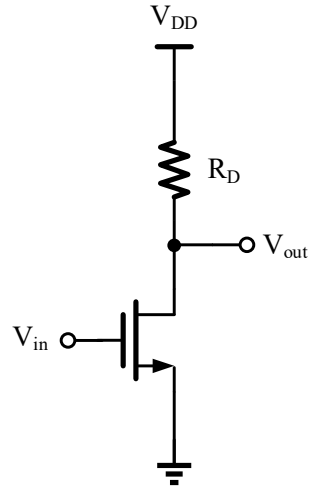


Figure 5.2

5.3 Consider the circuit of Fig 5.3 with $(W/L)_1 = 50/0.5$ and $(W/L)_2 = 10/0.5$. Assume that $\lambda = \gamma = 0$, $V_{DD} = 3\text{V}$.

- At what input voltage is M_1 at the edge of the triode region? What is the small-signal gain under this condition?
- When V_{out} is 0.66 V, what is the small-signal gain under this condition?

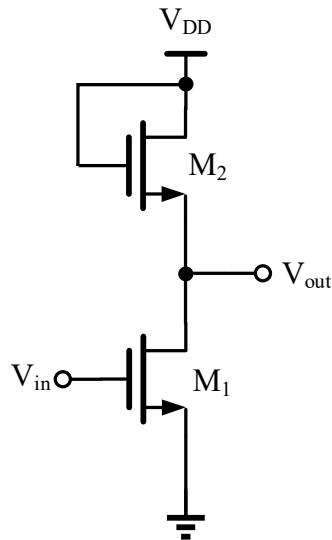


Figure 5.3

5.4 In the circuit of Fig 5.4, $(W/L)_1 = 20/0.5$, $I_1 = 1\text{mA}$, and $I_S = 0.75\text{mA}$. Assuming $\lambda = 0$, $V_{DD} = 3\text{V}$, calculate $(W/L)_2$ such that M_1 is at the edge of triode region. What is the small-signal voltage gain under this condition? Use model parameters in Table 5.1.

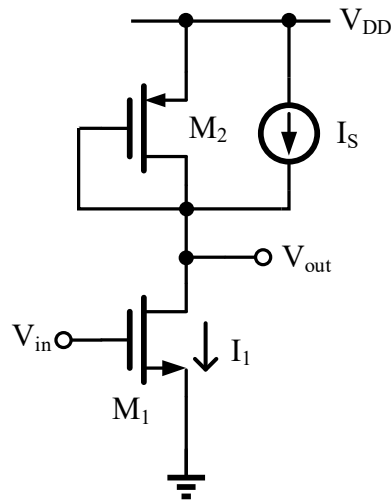


Figure 5.4

5.5 Consider the circuit of Fig 5.5 with $(W/L)_1 = 50/0.5$, $R_D = 2k\Omega$, and $R_S = 200\Omega$, $V_{DD} = 3V$.

Use model parameters in Table 5.1.

- Calculate the small-signal voltage gain if $I_D = 0.5mA$.
- Assuming that $\lambda = \gamma = 0$, calculate the input voltage that places M1 at the edge of the triode region. What is the gain under this condition?

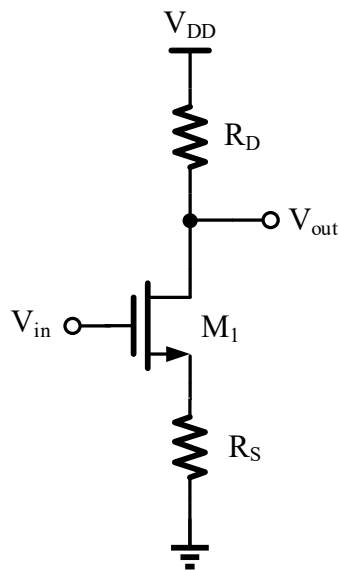


Figure 5.5